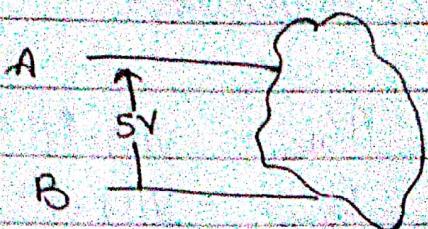


Current is a "through" variable

Potential is a "across" variable.




$$V_{BA} = +5V$$

$$V_{AB} = -5V$$


Power (P)

$$P(t) = V(t) \times i(t)$$

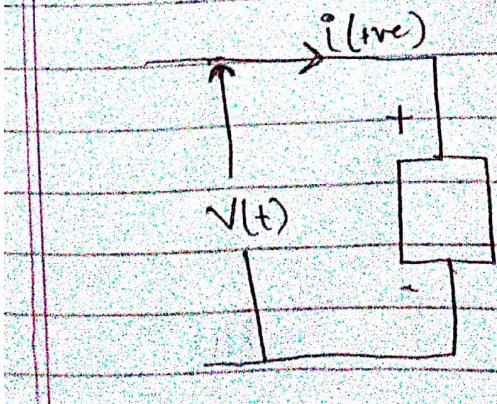A circuit component can be an absorber or a generator of power.



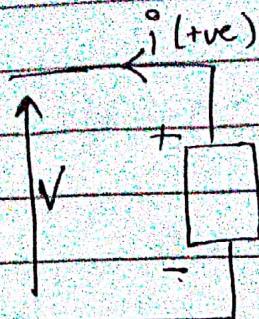If the situation is as this then the power is being absorbed.



Here power is being dissipated.

## Passive Sign Convention

$$P_{abs} = V(t) \times I(t) \quad (\text{it will be +ve})$$

$$P_{gen} = -V(t) \times I(t) \quad (\text{it will be -ve})$$




$$P = 2 \times 3 \text{ abs.}$$


$$\text{abs } -2 \times -3$$

## Voltage and Current Sources


Two types :- Independent  
Dependent

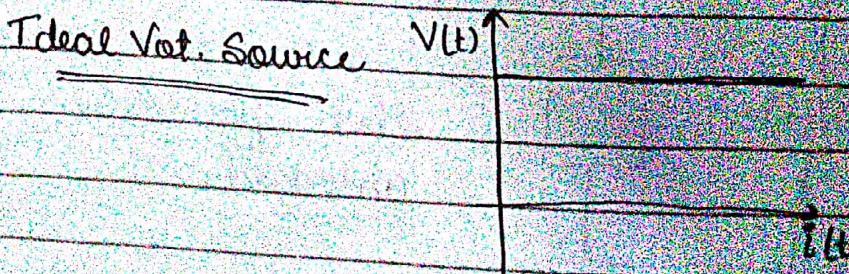


## Ideal Curv. Source

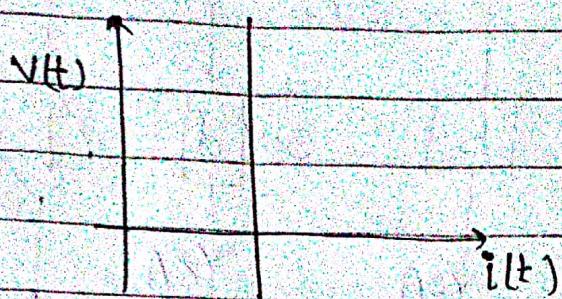

## Independent

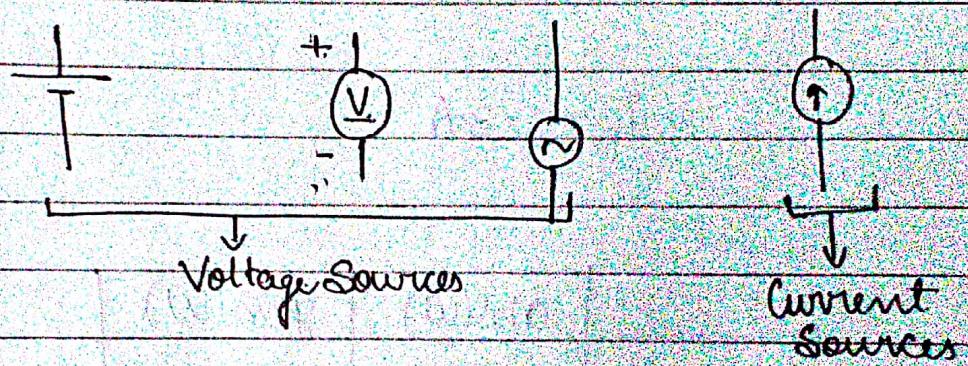


## Dependent Source

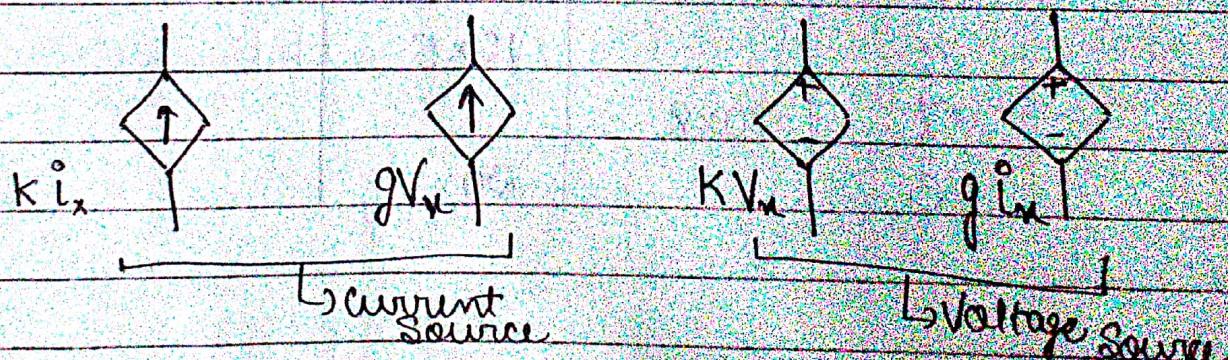

$K$  and  $g$  are const. with appr. dimensions

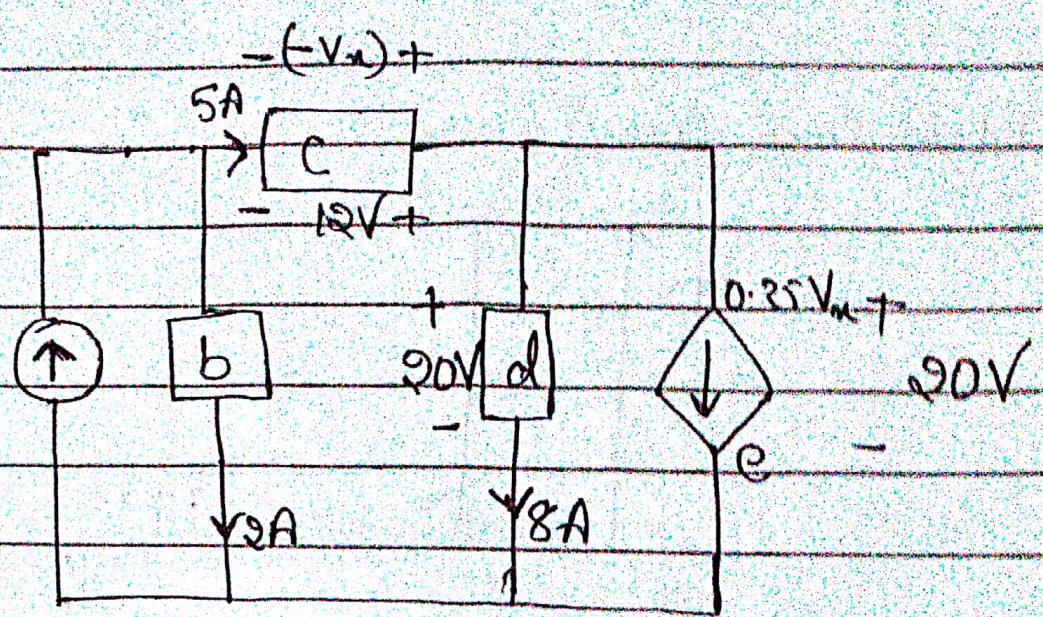So, the sources are dep. on either  $i$  or  $V$  and their values equal to a const. multiple of Vol. or cur.



$$i_e = 0.25V_m$$

$$-V_m = 12V$$

$$\Rightarrow V_m = -12V$$

$$\therefore i_e = -3A$$

	$abs(w)$	$gen(w)$
a		$7 \times 8$
b	$8 \times 2$	
c		$12 \times 5$
d	$20 \times 8$	
e		$20 \times 3$


## Ohm's Law

$$V \propto i$$


$$V = iR$$

$R$  - resistance ( $\Omega$ )

$$\underline{R = \rho l / A}$$

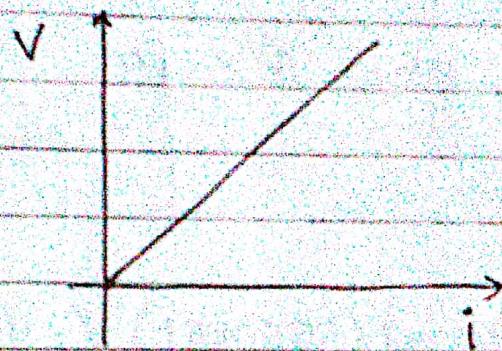


## Ideal Voltage Source

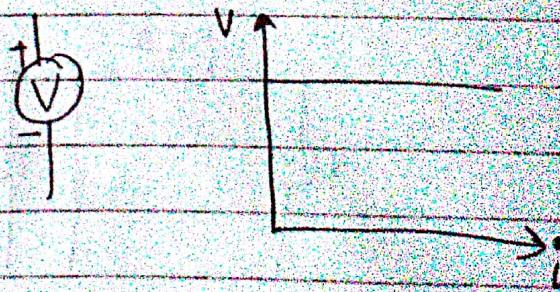
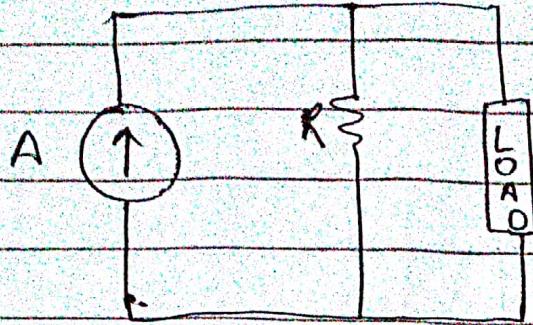
## Non Ideal

Non-ideal source <sup>is like</sup> has a Resist. in series with the voltage source.






For a curr. source,  $R$  would be in  $11^{\text{th}}$

Short Circuit  $\Rightarrow R \rightarrow 0$


Open Circuit  $\Rightarrow R \rightarrow \infty$

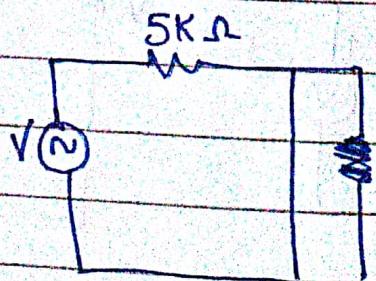Ques) A voltage source of  $(20\sin\pi t)$  V is connected across a  $5\text{k}\Omega$  res. Find the curr. through res. and power dissipated.



$$i = 4\sin\pi t \text{ mA}$$
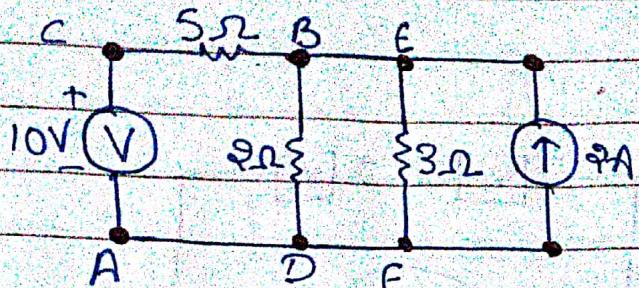
$$\text{Power (P)} = 80\sin^2\pi t \text{ mW}$$



→ Branches :- Eg:- BC, BD, EF etc.

→ Nodes :- Pt. with which all ~~other~~ components are connected with a shoot.


Eg:- A, B

→ Loop


KVL & KCL

KCL :-

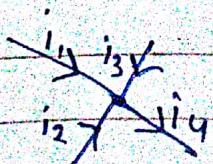
Sum of curr. coming at a pt. equal that leaving.



$$i_1 + i_2 + i_3 - i_4 = 0$$

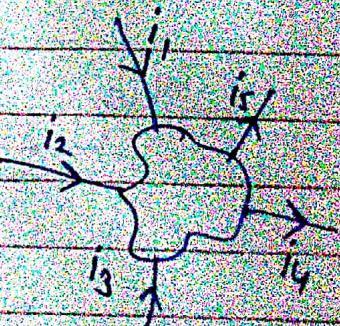


KVL

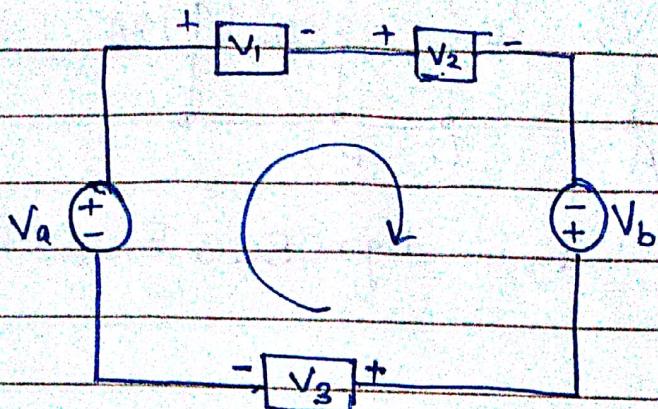

$$V_a - V_1 - V_2 + V_b - V_3 = 0$$


$$\Rightarrow \underline{V_a + V_b = V_1 + V_2 + V_3}$$

i)

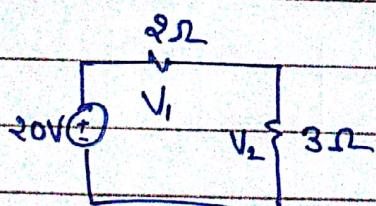


$$V_1 = 8V \quad V_2 = 12V$$

ii)

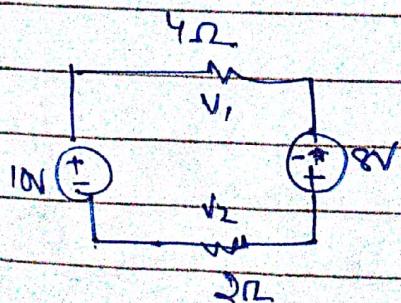

$$V_1 = 12V \quad V_2 = 6V$$

(Que)

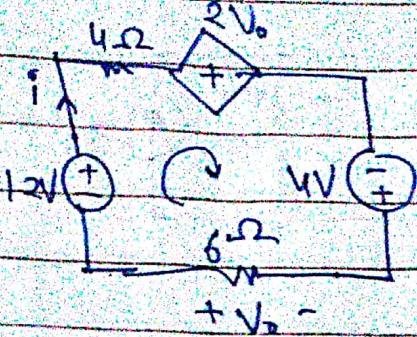

$$12 - 4i - 2V_o + 4 + V_o = 0$$

$$V_o = 6i$$


$$\Rightarrow 16 = 4i + V_o$$

$$16 = 22i$$

$$i = \cancel{8} / \cancel{11}$$

$$\therefore V_o = \cancel{48} / \cancel{11}$$

(Que)

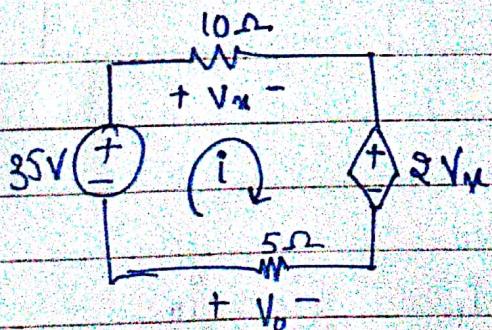

$$V_o = +5i$$

$$V_x = +10i$$


$$35 - 10i - 20i + 5i = 0$$

$$\Rightarrow \underline{\underline{i = 1A}}$$

$$\therefore V_o = 5V$$

$$V_x = 10V$$

Ques

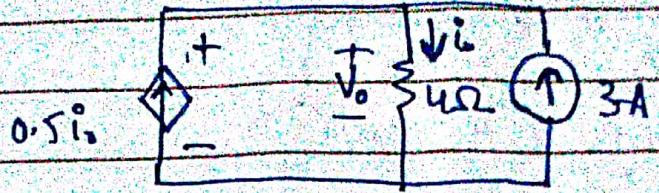


$$3 - i_o + 0.5 i_o = 0$$

$$\Rightarrow \underline{i_o = 6A}$$

$$V_o = \cancel{8} 4A$$

$$P_{gen} = V_o \times 0.5 i_o$$

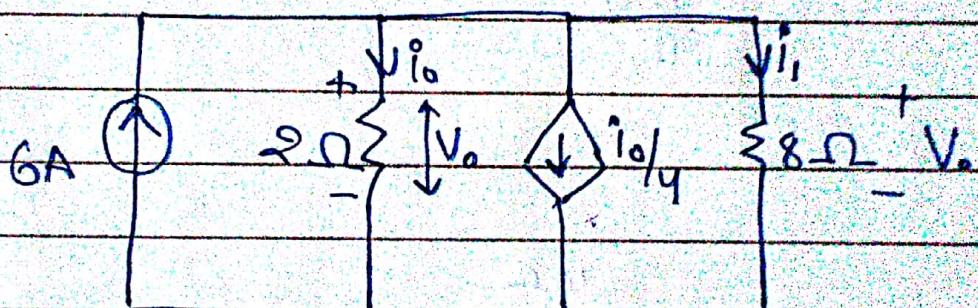


$$2 i_o = V_o$$


$$\Rightarrow i_1 = \frac{2 i_o}{8} = \frac{i_o}{4}$$

$$\therefore 6A = \frac{3 i_o}{2}$$

$$\underline{i_o = 4A}$$

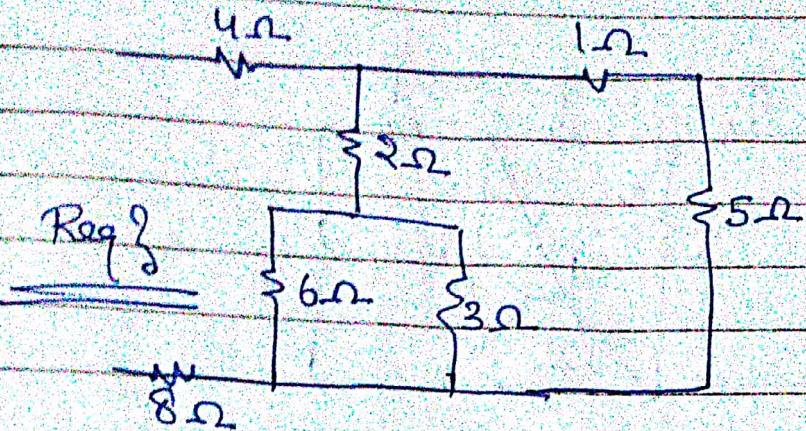(Ques)


Req?

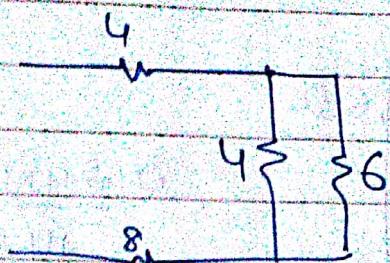Ans


$$\begin{aligned} R_{eq} &= 4 + 8 + 2 \cdot 4 \\ &= 14 \text{ ohm} \end{aligned}$$

$$\frac{18}{9} \text{ ohm}$$

$$\frac{24}{10} \text{ ohm}$$



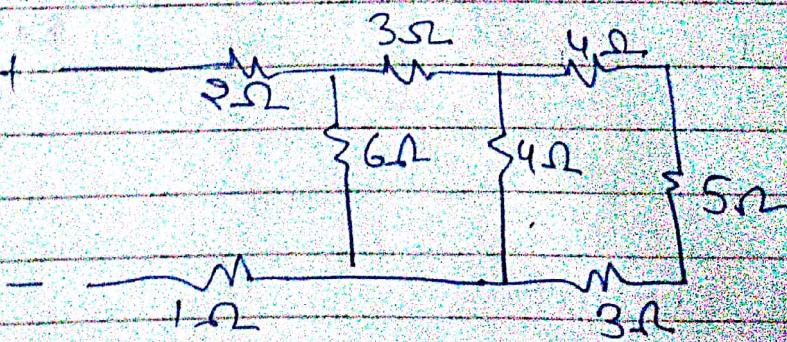
(Ques)

Req?

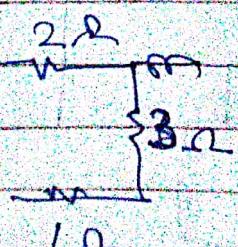




$$= R_{eq} = 6 \text{ ohm}$$

(Ans)

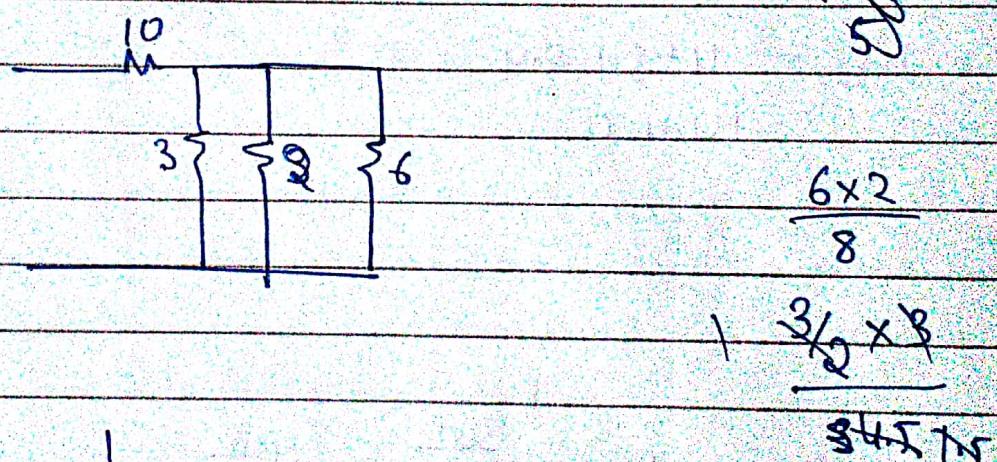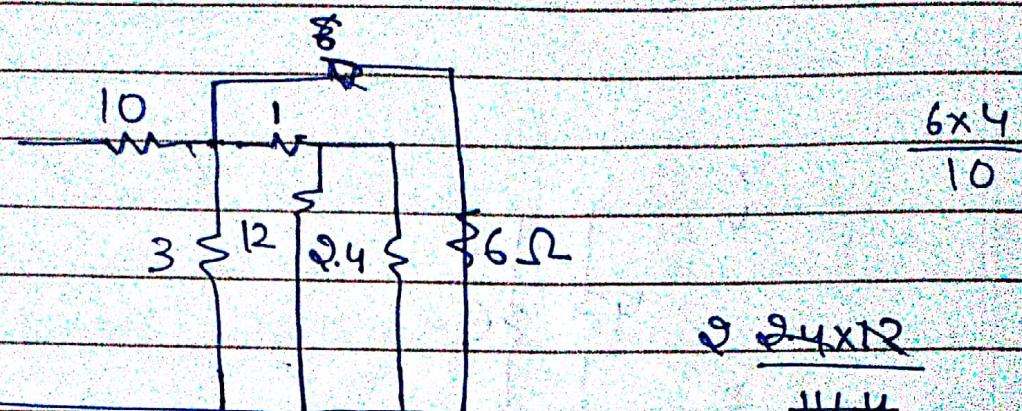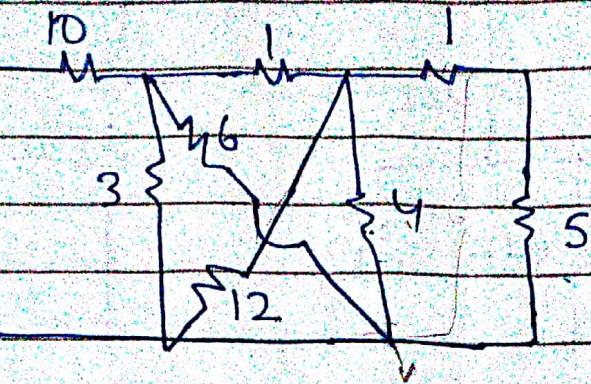

eql. circuit

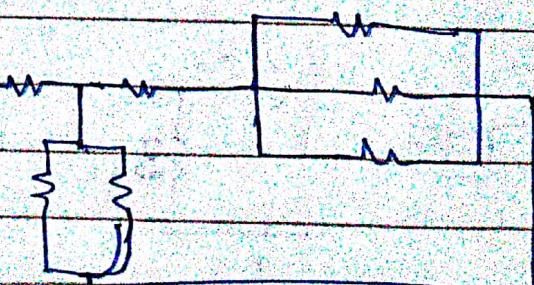

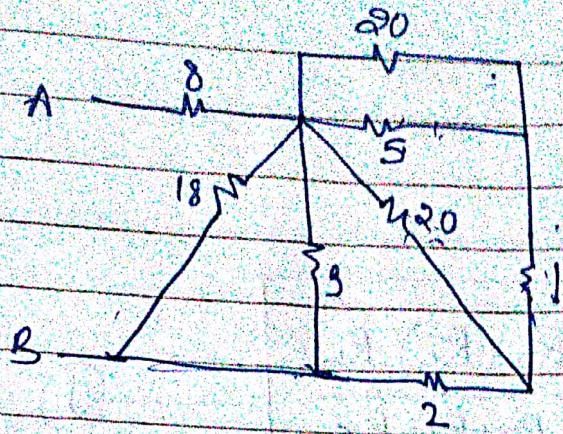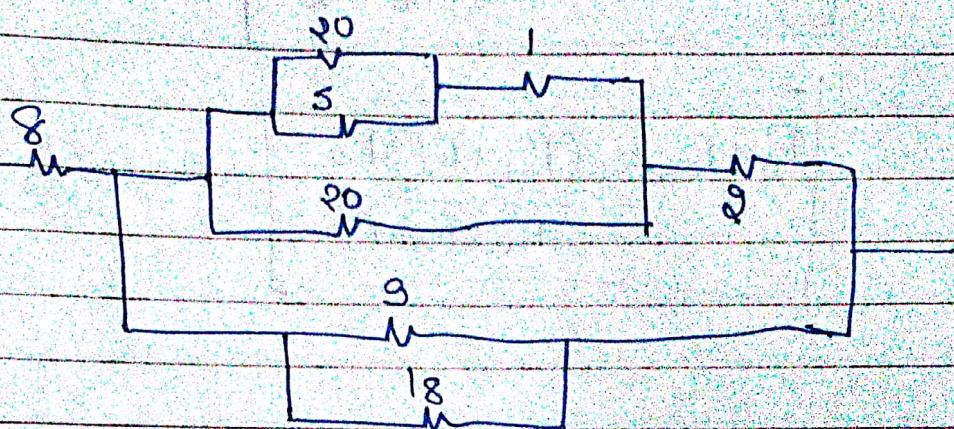
(Ans)Ans

$$R_{eq} = 11 \Omega$$

$$\frac{90 \times 5}{25} = 4$$

$$\frac{6 + 8 \times 9}{27} \Omega$$

When Subst. ~~R<sub>P</sub>~~ a network with the star network.

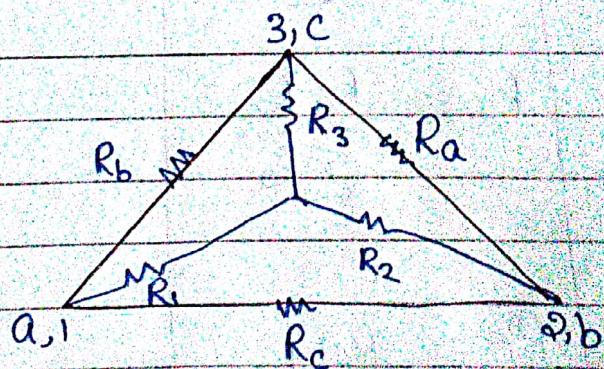(Ans)

$$\underline{R_{12}} = \underline{R_{ab}}$$

$$R_1 + R_2 = R_c || R_a + R_b$$

$$\frac{R_1 + R_2}{R_1 + R_2 + R_c} = \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} \quad (1)$$

Similarly

$$R_{13} = R_{ac}$$

$$R_1 + R_3 = \frac{(R_a + R_c) R_b}{R_a + R_b + R_c}$$

④

$$R_2 + R_3 = \frac{(R_b + R_c) R_a}{R_a + R_b + R_c}$$

⑤

$$\textcircled{1} - \textcircled{5} \Rightarrow \textcircled{4} \Rightarrow R_1 - R_3 = \frac{R_b R_c - R_a R_b}{\sum R_a}$$

$$\textcircled{4} + \textcircled{4} \Rightarrow R_1 = \frac{R_b R_c}{\sum R_a}$$



$$R_2 = \frac{R_a R_c}{\sum R_a}$$

$$R_3 = \frac{R_a R_b}{\sum R_c}$$

$$R_a = \frac{\sum R_1 R_2}{R_1}$$

$$R_b = \frac{\sum R_1 R_2}{R_2}$$



$$R_c = \frac{\sum R_1 R_2}{R_3}$$

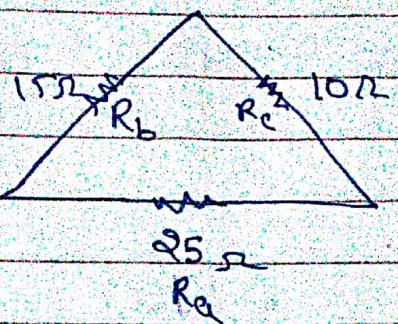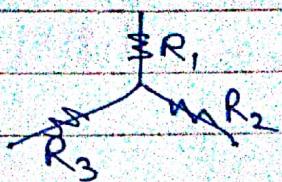(Ques)(Ans)

$$R_1 = \frac{150}{50} = 3$$

$$R_2 = \frac{250}{50} = 5 \Omega$$

$$R_3 = \frac{375}{50} = 7.5 \Omega$$

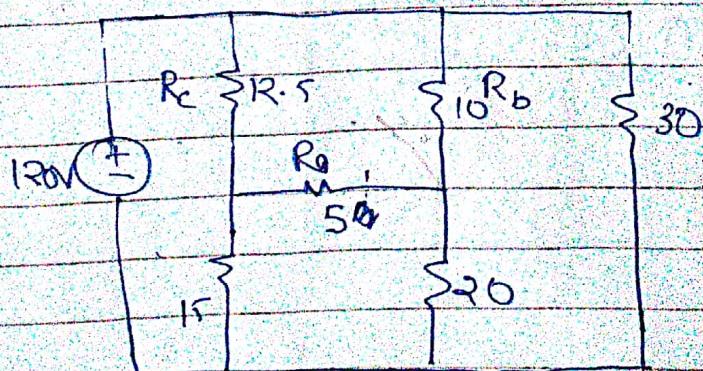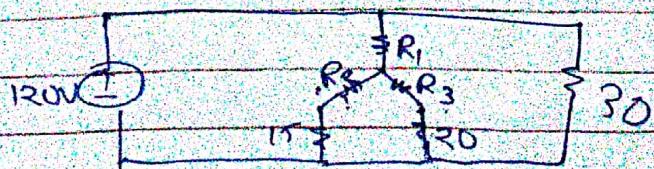(Ques)(Ans)

$$R_1 = \frac{125}{27.5} = 4.5454$$

$$R_2 = \frac{62.5}{27.5} = 2.2727$$

$$R_3 = \frac{500}{27.5} = 1.8181$$

$$R_{\text{req}} = \frac{(R_2 + 15)(R_3 + 20)}{R_1 + R_2 + 35}$$

$$= \frac{(17.2727)(21.8181)}{R_1 + R_2 + 35}$$

$$= \cancel{5.0864} \quad 9.6408$$

$$\therefore R_{\text{req}} = 9.632 \Omega$$


# Nodal Analysis

KCL


$n$  — "node" ( $n$  no. of nodes)

ref-node


datum/ground

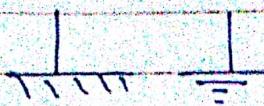

(ans))

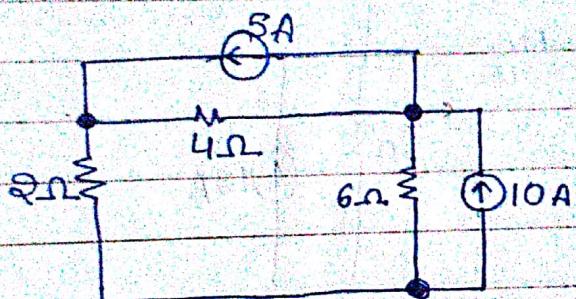

(ans))

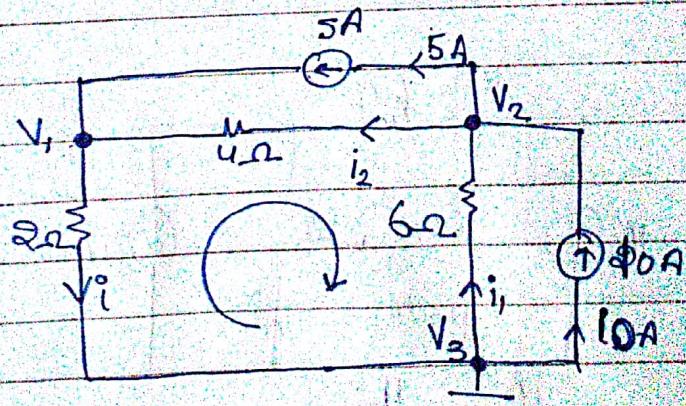

$$V_3 = 0$$

$$i_2 + 5 = i_1 \quad | \quad i_1 + 10 = i$$

~~$$V_2 - V_3 = -6i_1$$~~

$$\begin{aligned} & 2i + 4i_2 + 6i_1 = 0 \\ & \Rightarrow 2i + 4(i-5) + 6(1-10) = 0 \\ & \Rightarrow 12i = 80 \Rightarrow i = 20/3 \end{aligned}$$

$$i = 6.66A$$


$$i_1 = -10/3A \quad i_2 = \frac{+10}{3}A$$

$$V_1 = 2i = 40/3V$$

$$V_2 = 20V$$


$$\frac{10}{3}x$$

(One)

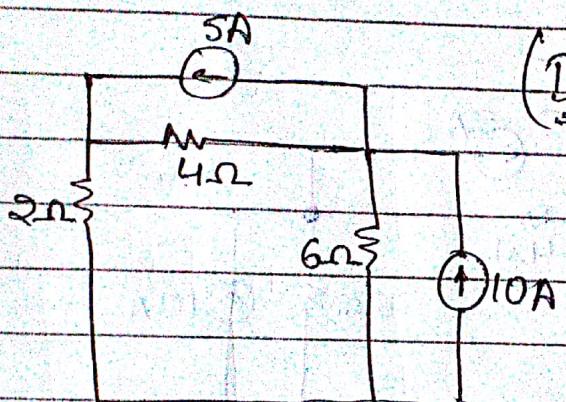

(Done above)

(One)

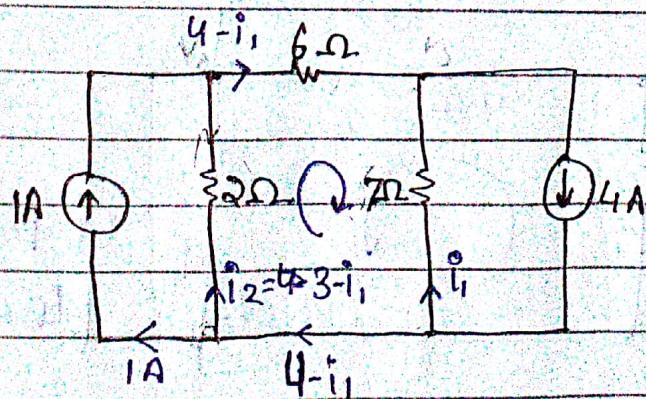

(Ans)


$$\Rightarrow (i_1 - 4)6 + 7i_1 + (i_1 - 3)2 = 0$$

$$\Rightarrow 6i_1 + 7i_1 + 2i_1 = 24 + 6$$


$$15i_1 = 30$$

$$\underline{i_1 = 2A}$$

(Ques)

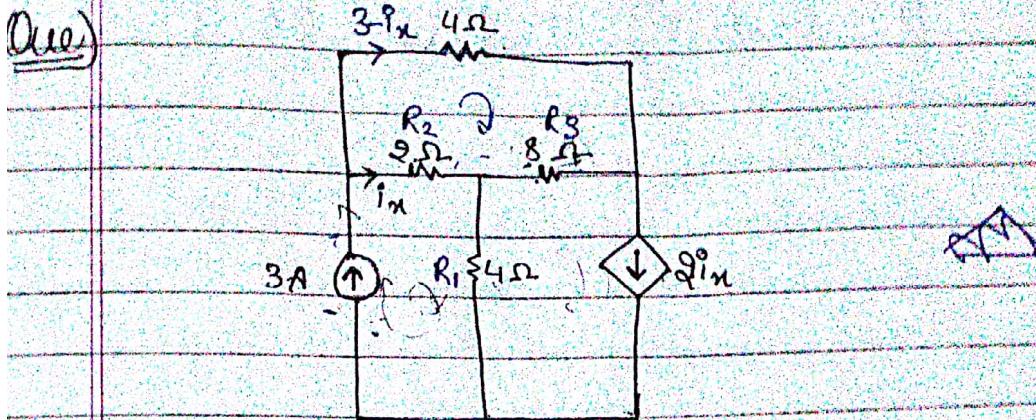

Ans)

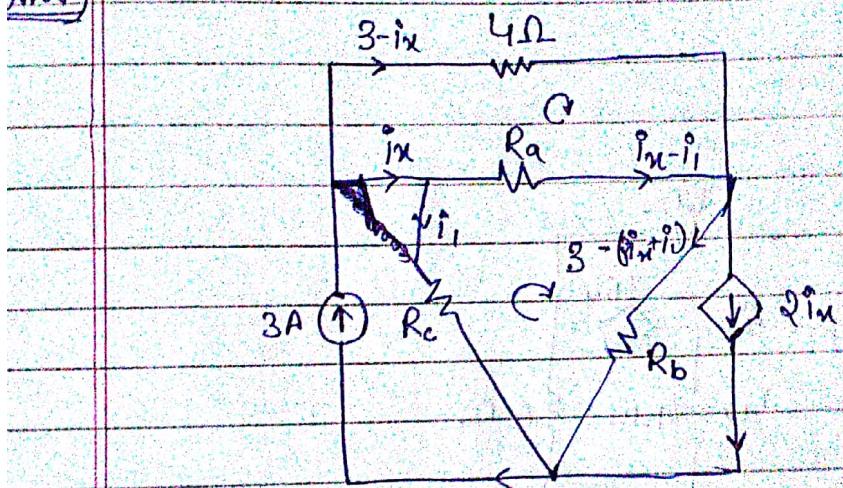

$$R_a = \frac{8 + 32 + 16}{4} = 14 \Omega$$

$$R_b = \frac{56}{2} = 28 \Omega$$



$$R_c = \frac{56}{8} = 7 \Omega$$

$$-4(3 - i_n) + (i_n - i_1)14 = 0 \\ \Rightarrow 5i_n - 14i_1 = 12 \quad (1)$$


$$(i_n - i_1)(-14) + \{2(i_n + i_1) - 3\} 28 + 7i_1 R_c = 0$$

$$14i_1 + 28i_1 - 14i_n + 56i_n + 7i_1 - 84 = 0$$
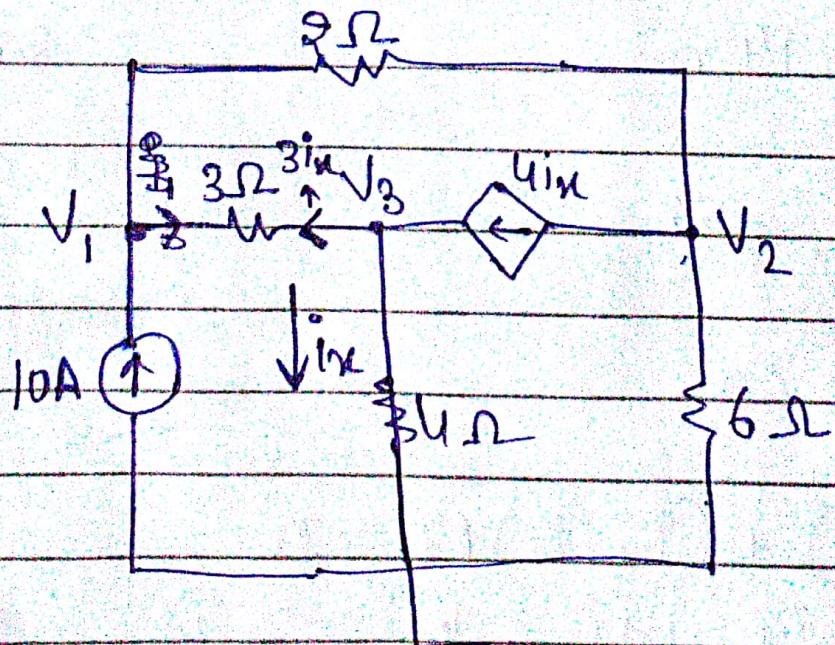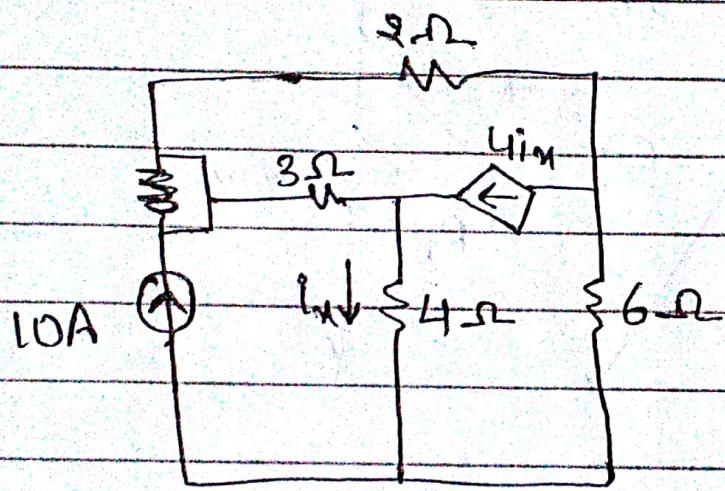
$$49i_1 + 42i_n - 84 = 0 \Rightarrow 7i_1 + 6i_n = 12 \quad (2)$$



(Ques)

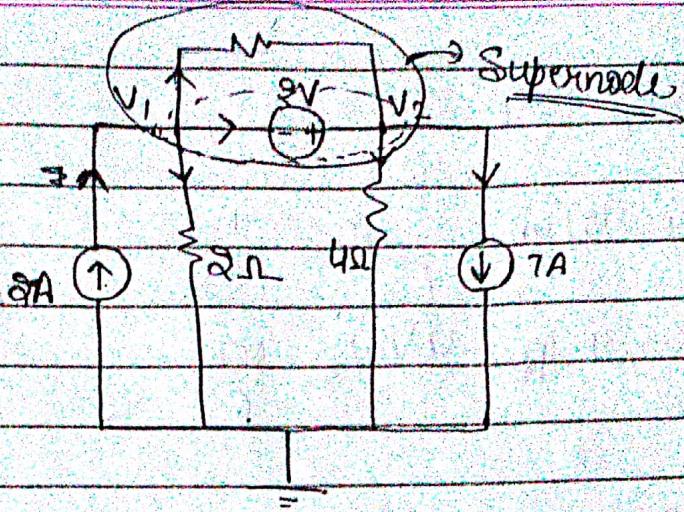


$$\vartheta = \frac{V_1}{3} + \frac{V_2}{4} + 7 \quad \textcircled{1}$$

$$V_2 = V_1 + \vartheta \quad \textcircled{2}$$

$$V_1 = -6V - 22/3 V$$

$$V_2 = -8V - 16/3 V$$

(Ques)

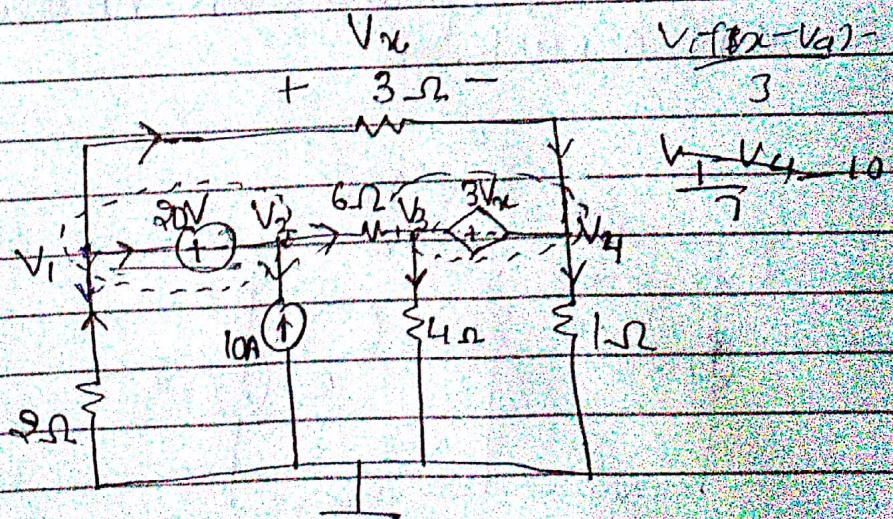

$$V_1 - V_2 = 20V$$

$$V_3 - V_4 = 3(V_1 - V_4) \quad (V_1 - V_4)$$

$$V_1 - V_4 = 3V_2 - V_{ax}$$

KCL along nodes


$$\frac{V_1}{2} + 10 = \frac{V_1 - V_4}{3}$$

$$\frac{V_1 - 20 - V_3}{6} + \frac{V_1 - V_4}{3} = \frac{V_3}{4} + \frac{V_4}{1}$$

## Mesh Analysis

A loop which has no other loop is called a mesh.

(One)

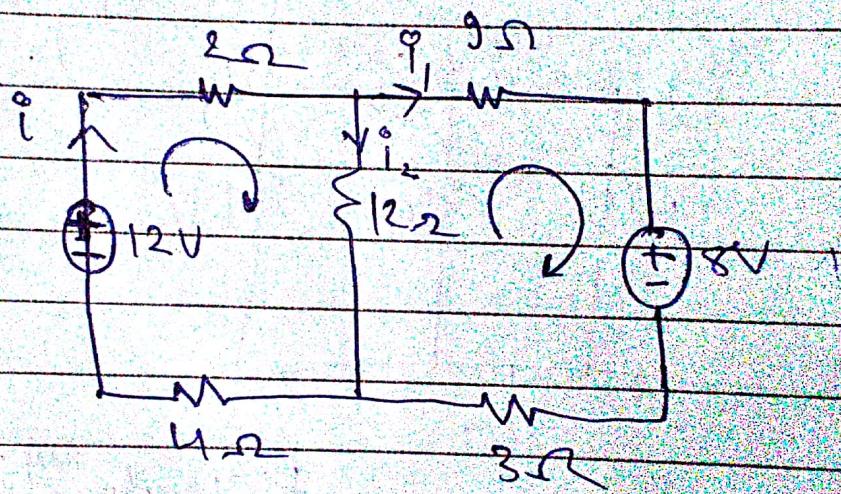


$$\text{KVL} \quad -2i - 12i_2 - 4i + 12 = 0$$

$$i_2 = 9 - i_1$$

$$\Rightarrow \frac{6 = i + 6i - 6i_1 + 9}{6 = 9i - 6i_1} \quad | 2 = 3i - 2i_1$$

Ques)

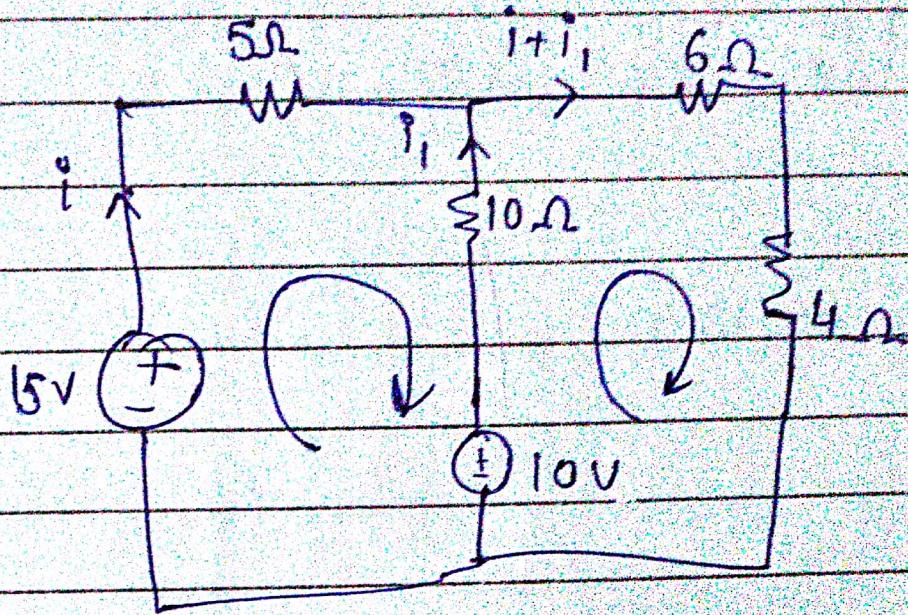

Sols


$$15 - 5i + 10i_1 - 10 = 0$$

$$\boxed{5i - 10i_1 = 5} \Rightarrow \boxed{1i - 2i_1 = 1}$$


$$-(i + i_1)6 - 4(i + i_1) + 10 - 10i_1 = 0$$

$$10(i + i_1) + 10i_1 = 170$$
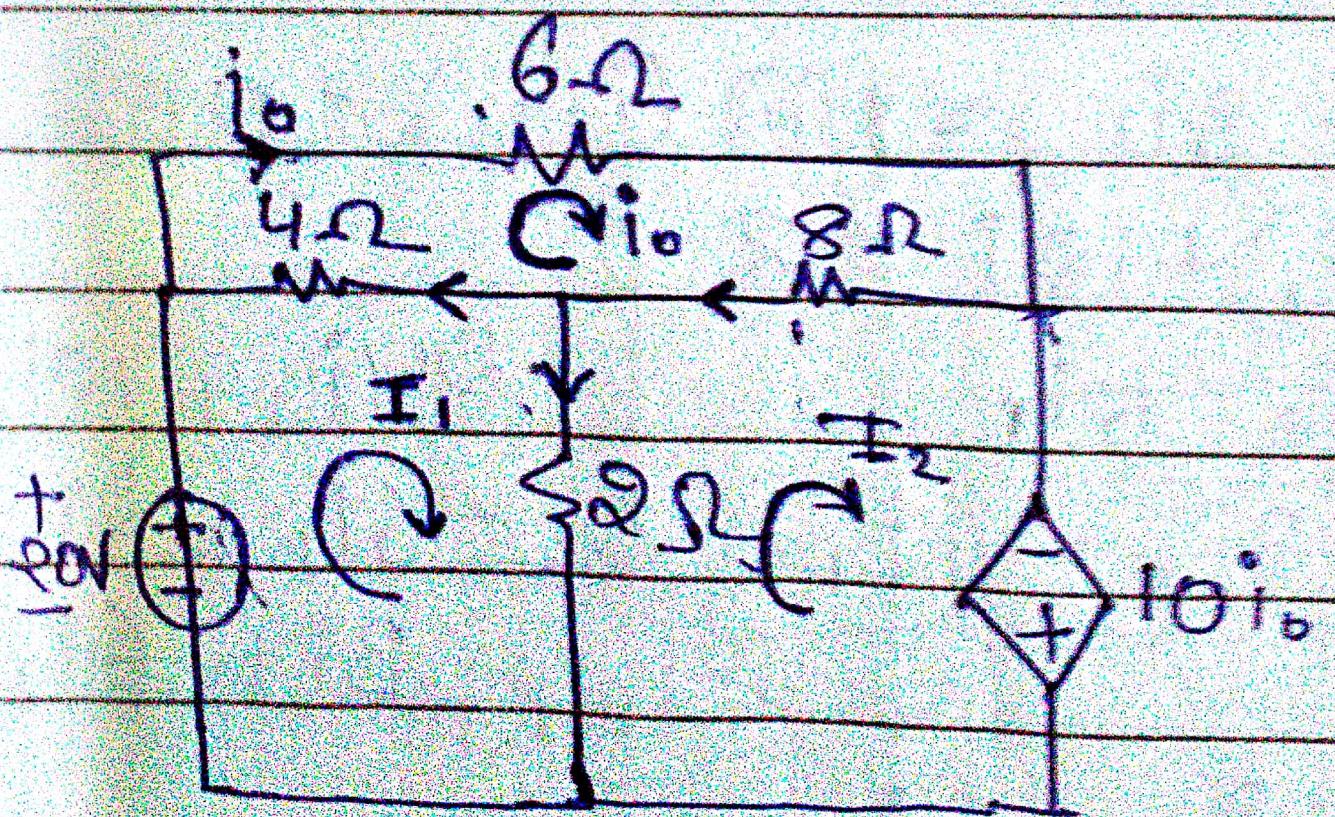
$$\boxed{10i_1 + i = 17} \Rightarrow \underline{i = 1A} \quad \underline{i_1 = 0}$$




Date

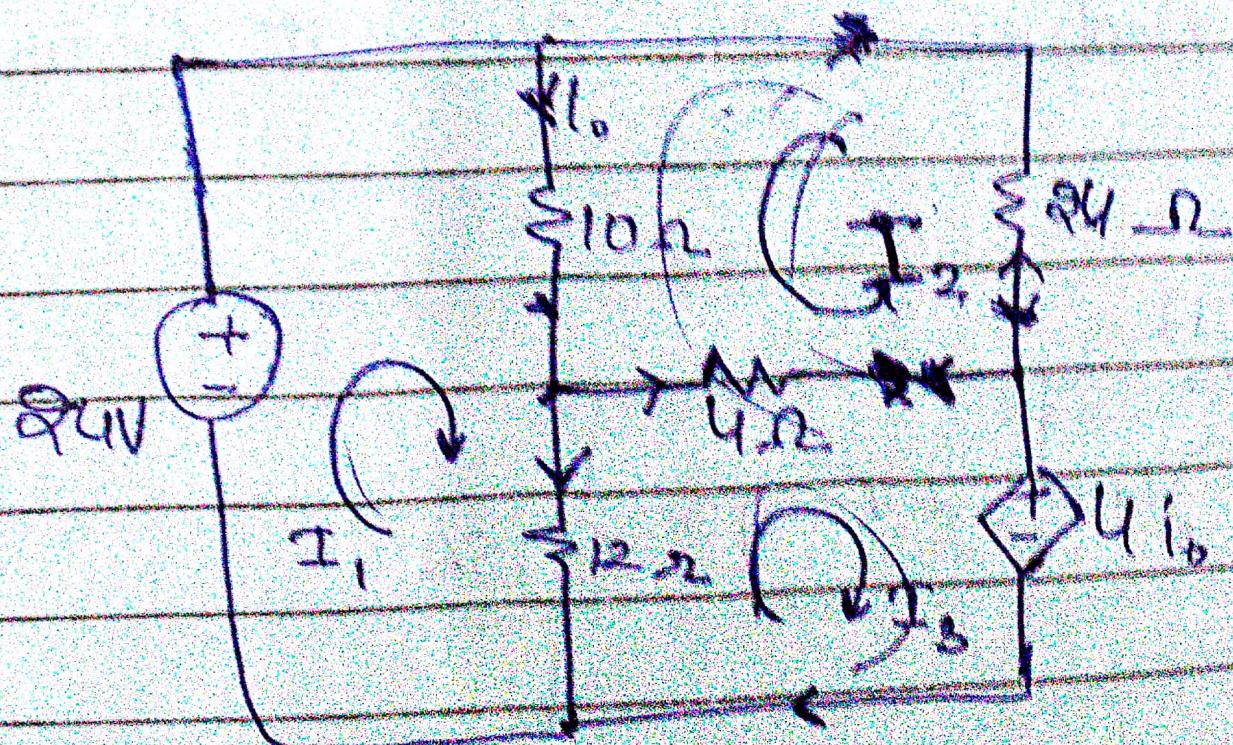

# Mesh Analysis with Current Sources

(1)

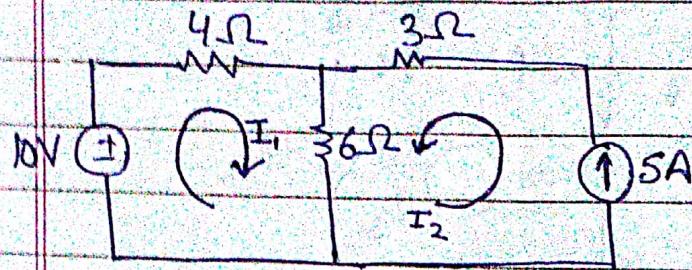

Here  $I_2 = 5A$


$$10V - 4I_1 - 6(I_1 + I_2) = 0$$

$$\Rightarrow 10 - 10I_1 - 30 = 0$$

$$\Rightarrow \frac{-20}{10} = I_1$$

$$\Rightarrow I_1 = -2A$$

(2)

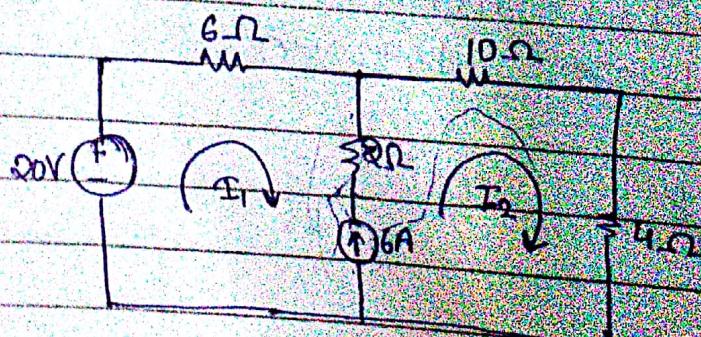

Here we will apply KVL for the bigger loop and  
to the intermed. branch is connected wif

$$I_1 - I_2 = 6A$$


$$20 - 6I_1 - 10I_2 - 4I_2 = 0$$

$$20 = 6I_1 + 14(I_1 + 6) \Rightarrow$$

$$20 + 84 = 20I_1$$

$$\frac{104}{20} = I_1 \Rightarrow \cancel{-5.2A} - 3.2A = 1$$

Ques)

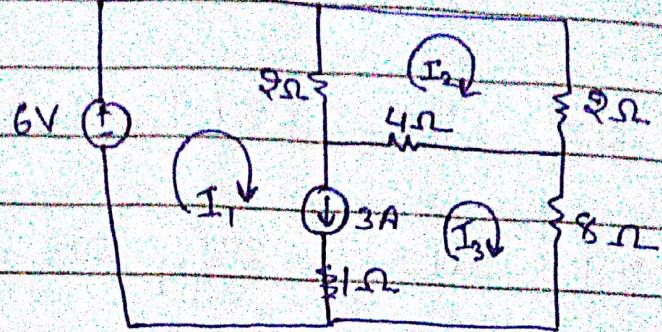

$$I_1 - I_3 = 3 \text{ A} \quad \textcircled{1}$$

$$\begin{aligned} 2(I_1 - I_2) - 2I_2 + 4(I_3 - I_2) &= 0 \\ \Rightarrow 2I_1 - 8I_2 + 4I_3 &= 0 \quad \textcircled{2} \end{aligned}$$

Superloop


$$6V - 2I_2 - 8I_3 = 0 \quad \textcircled{3}$$

$$I_1 = \frac{30}{19} \quad 66/19$$

$$I_2 = \frac{9}{19} \quad 9/19$$

$$I_3 = \frac{3}{19} \quad 9/19$$

Ques)

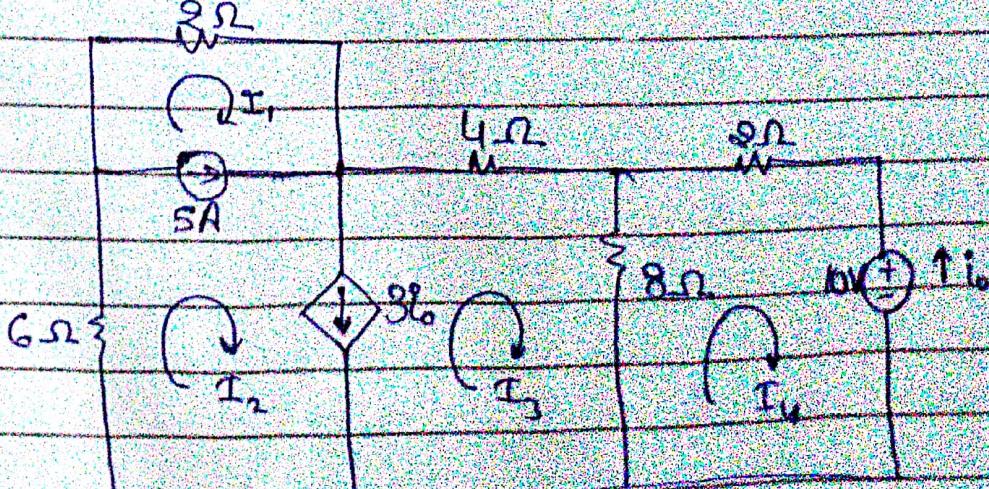


$$-I_2 + I_3 = -3I_6 \quad \textcircled{1} \quad I_4 = -I_6 \quad \textcircled{2}$$

$$\Rightarrow 3(I_4 - I_2) - 2I_4 - 10 = 0$$

$$\Rightarrow 6I_4 - 8I_2 = 10 \quad \textcircled{3} \quad \Rightarrow -8I_2 - 10I_4 = 10 \quad \textcircled{4}$$


# Source Transformation

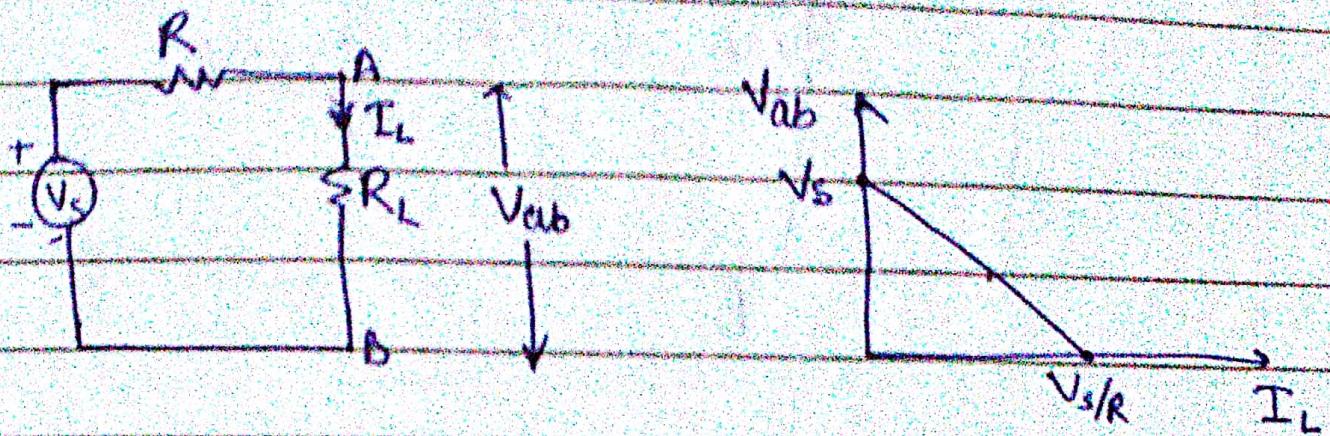

$$\text{i) } R_L = 0 \Rightarrow V_{ab} = V_s / R$$


$$V_{ab} = 0$$
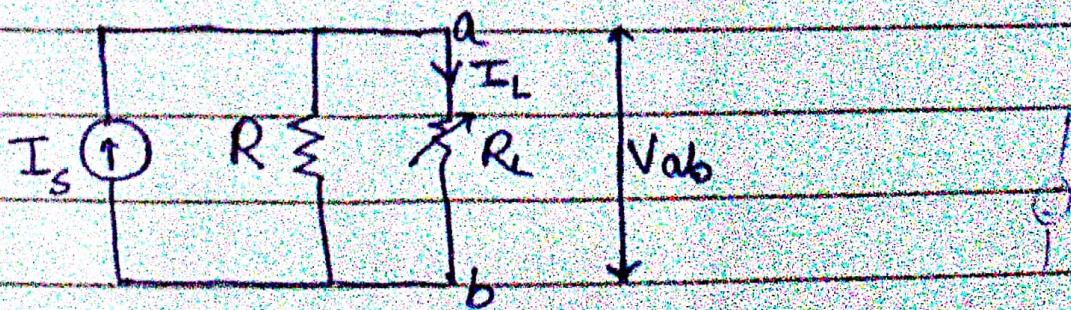
$$\text{ii) } R_L \rightarrow \infty ; V_{ab} \rightarrow V_s ; I_L \rightarrow 0$$








$$\text{i) } R_L = 0 , V_{ab} = 0 , I_L = I_s$$
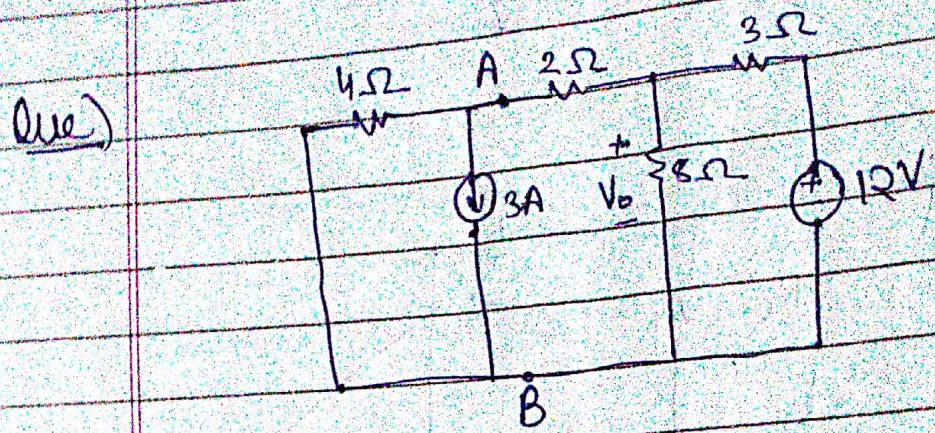
$$\text{ii) } R_L \rightarrow \infty , V_{ab} = I_s R , I_L \rightarrow 0$$










Ans

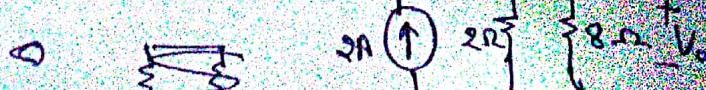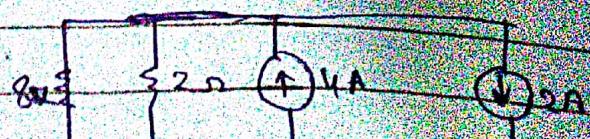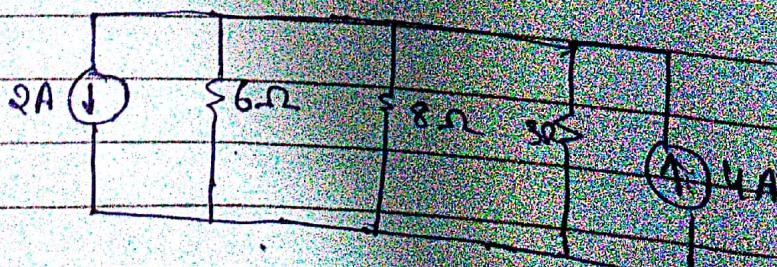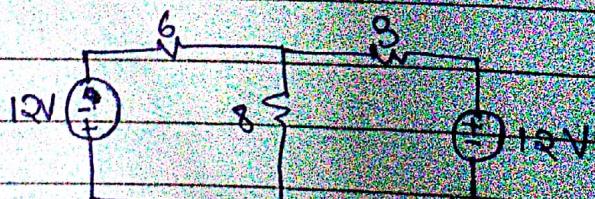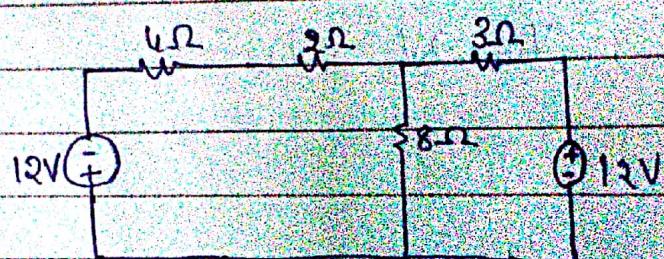↪ Replace curr. source with a volt. source


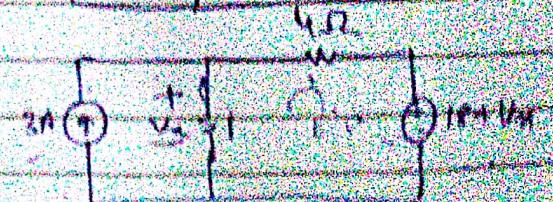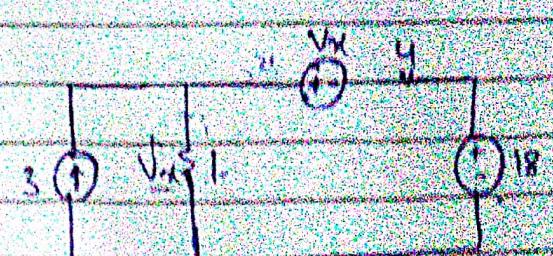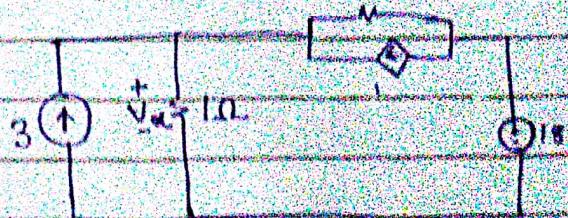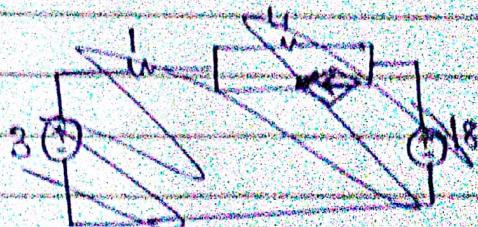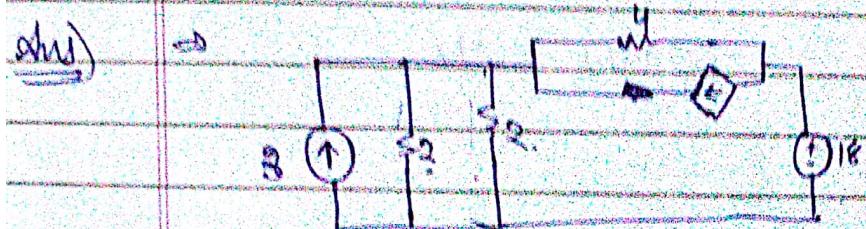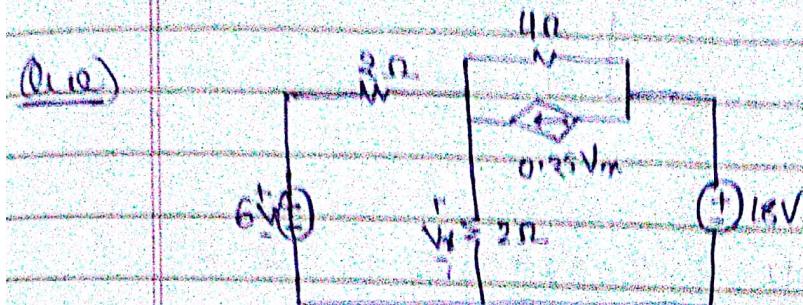
$$\text{so } V_d = 1.6 \times 2 = 3.2 \text{ V}$$



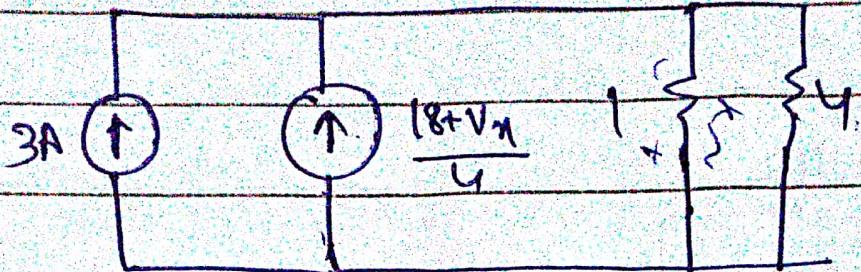

$$V_m = \frac{4}{5} \times \left( 3 + \frac{18 + V_m}{4} \right)$$

$$\frac{30 + V_m}{5} = V_m$$

$$\frac{30}{4} = V_m$$